



K. J. Somaiya College of Engineering, Mumbai-77

Experiment / Assignment / Tutorial No. 2

Grade: AA / AB / BB / BC / CC / CD / DD

Signature of the Staff In-charge with date



K. J. Somaiya College of Engineering, Mumbai-77

Batch: B1

Roll No.: 1711072

Experiment / assignment / tutorial No.: 2

Title: Binary Adders and Subtractors

Objective: To implement half and full adder–subtractor using gates and IC 7483

Expected Outcome of Experiment:

CO2: Use different minimization technique and solve combinational circuits, synchronous & asynchronous sequential circuits.

Books/ Journals/ Websites referred:

- R. P. Jain, “Modern Digital Electronics”, Tata McGraw Hill
- M .Morris Mano, “Digital Logic & computer Design”, PHI
- http://physics.niser.ac.in/labmanuals/sem5/elect/7_ADDER%20SUBTRACTOR%20CIRCUITS.pdf

Pre Lab/ Prior Concepts:

Adder: Addition of two binary digits is most basic operation performed by the digital computer. There are two types of adder:

- Half adder
- Full adder

Half Adder: Half adder is combinational logic circuit with two inputs and two outputs. It is the basic building block for addition of two single bit numbers.

Full adder: A half adder has a provision not to add a carry coming from the lower order bits when multi bit addition is performed. for this purpose a third input terminal is added and this circuits is to add A,B,C where A and B are the nth order bits of the number A and B respectively and C is the carry generated from the addition of (n-1) order bits. This circuit is referred to as full adder.



K. J. Somaiya College of Engineering, Mumbai-77

Subtractor: Subtraction of two binary digits is one of the most basic operations performed by digital computer. There are two types of subtractor:

- Half subtractor
- Full subtractor

Half subtractor: Logic circuit for the subtraction of B from A where A, B are 1 bit numbers is referred to as half subtract or. The subtract or process has two input and difference and borrow are the two outputs.

Full subtractor: As in the case of the addition using logic gates, a full subtractor is made by combining two half-subtractors and an additional OR-gate. A full subtractor has the borrow in capability (denoted as BOR_{IN}) and so allows cascading which results in the possibility of multi-bit subtraction.

IC 7483

For subtraction of one binary number from another, we do so by adding 2's complement of the former to the latter number using a full adder circuit.

IC 7483 is a 16 pin, 4-bit full adder. This IC has a provision to add the carry output to transfer and end around carry output using Co and $C4$ respectively.

2's complement: 2's complement of any binary no. can be obtained by adding 1 in 1's complement of that no.


e.g. 2's complement of $+(10)_{10} = 1010$ is

$$\begin{array}{r} \text{1C of } 1010 \qquad 0101 \\ + \quad 1 \\ \hline -(10)_{10} \qquad 0110 \end{array}$$

In 2's complement subtraction using IC 7483, we are representing negative number in 2's complement form and then adding it with 1st number.


Implementation Details:

Half Adder Block Diagram

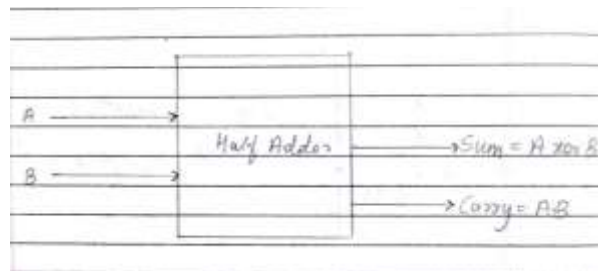

K. J. Somaiya College of Engineering, Mumbai-77

Half Adder Circuit

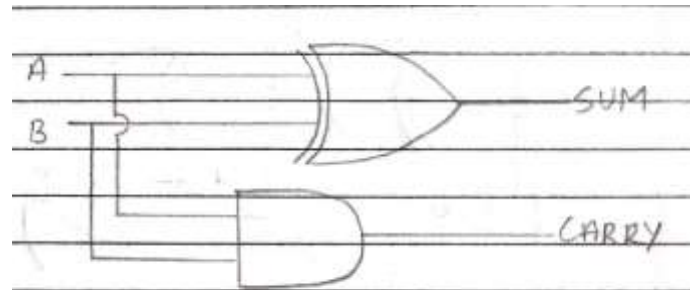

Truth Table for Half Adder


Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

From the truth table (with steps):

$$S = A.B' + A'.B$$


$$C = A.B$$

Full Adder Block Diagram

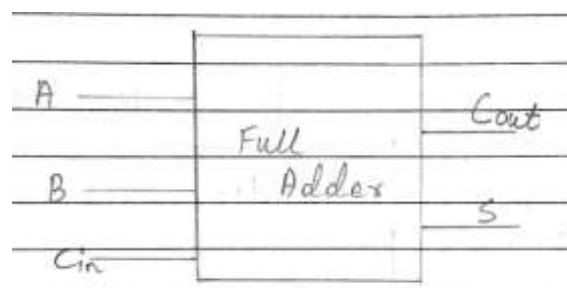

K. J. Somaiya College of Engineering, Mumbai-77

Full Adder Circuit

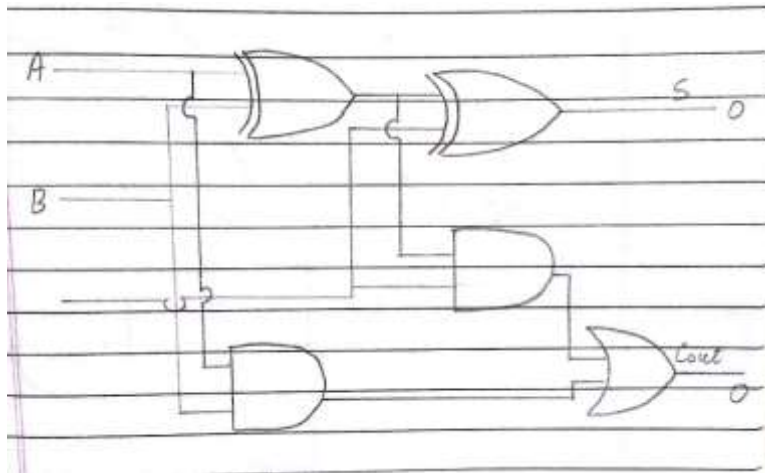

Truth Table for Full Adder

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


From the truth table (with steps):

$$S = A'.B'.C_{in} + A'.B.C_{in}' + A.B'.C_{in}' + A.B.C_{in}$$


$$C_{out}(\text{Carry}) = A.C_{in} + A.B + B.C_{in}$$

K. J. Somaiya College of Engineering, Mumbai-77

Half Subtractor Block Diagram

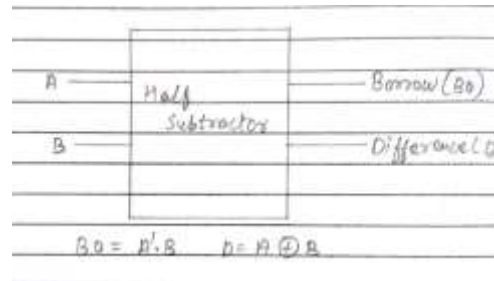

Half Subtractor Circuit

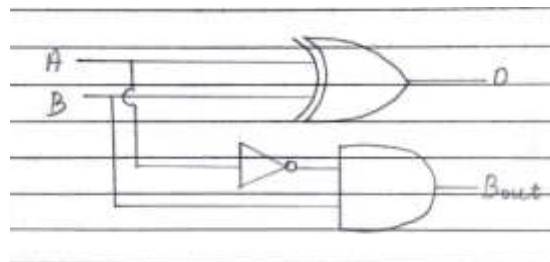

Truth Table for Half Subtractor

A	B	DIFFERENCE (D)	BORROW(Bo)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0


K. J. Somaiya College of Engineering, Mumbai-77

From the truth table (with steps) :


$$\text{Difference}(D) = A' \cdot B + A \cdot B'$$

$$\text{Borrow}(B_o) = A' \cdot B$$

Full Subtractor Block Diagram

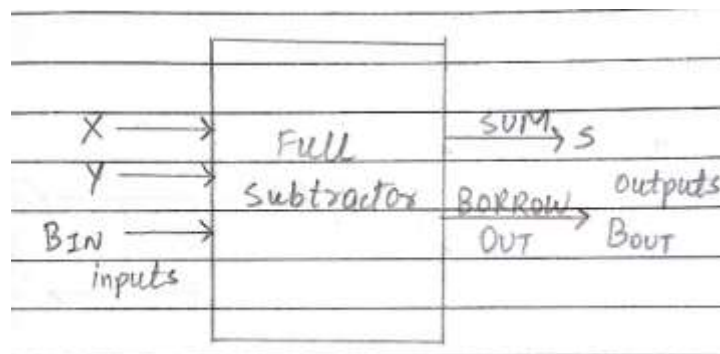

Full Subtractor Circuit

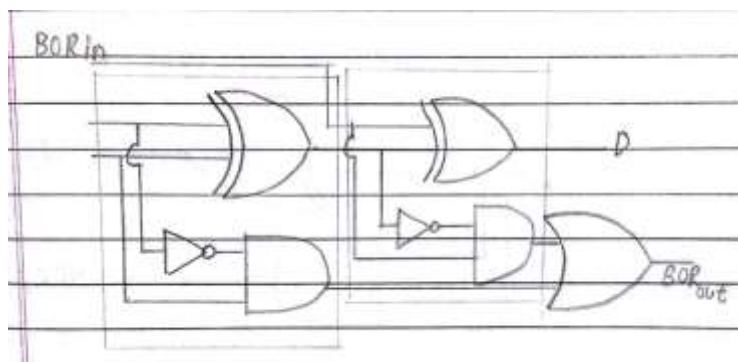



K. J. Somaiya College of Engineering, Mumbai-77

Truth Table for Full subtractor:

A	B	B _{IN}	D	BOR _{OUT}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

From the truth table (with steps):

$$\text{Difference (D)} = A'.B'.B_{in} + A'.B.B_{in}' + A.B'.B_{in}' + A.B.B_{in}$$

$$\text{BOR}_{out} = A'.B + A'.B_{in} + B.B_{in}$$

IC 7483

Procedure:

- 1) Locate the IC 7483 and 4-not gates block on trainer kit.
- 2) Connect 1st input no. to A4-A1 input slot and 2nd (negative) no. to B4-B1 through 4-not gates (1C of 2nd no.)
- 3) Connect high input to C₀ so that it will get added with 1C of 2nd no. to get 2C.
- 4) Connect 4-bit output to the output indicators.
- 5) Switch ON the power supply and monitor the output for various input combinations.

K. J. Somaiya College of Engineering, Mumbai-77

Example:

1) $7_{10} - 2_{10} = 5_{10}$

7 0111

2 0010

1's C of 2 1101

+ 1


2's C of 2 1110

0111


+ 1110

0101

Pin Diagram IC7483

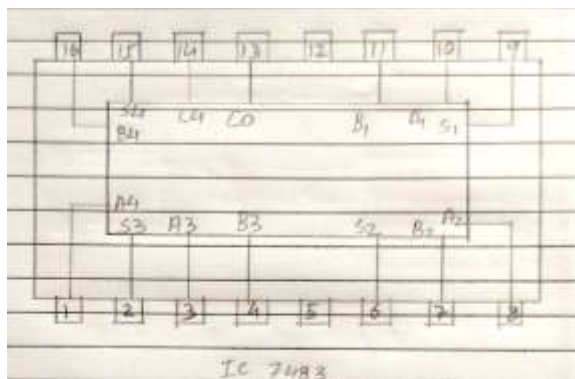


Adder

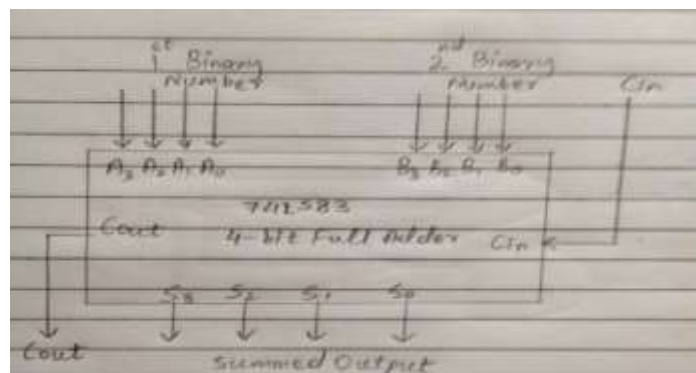

K. J. Somaiya College of Engineering, Mumbai-77

Subtractor

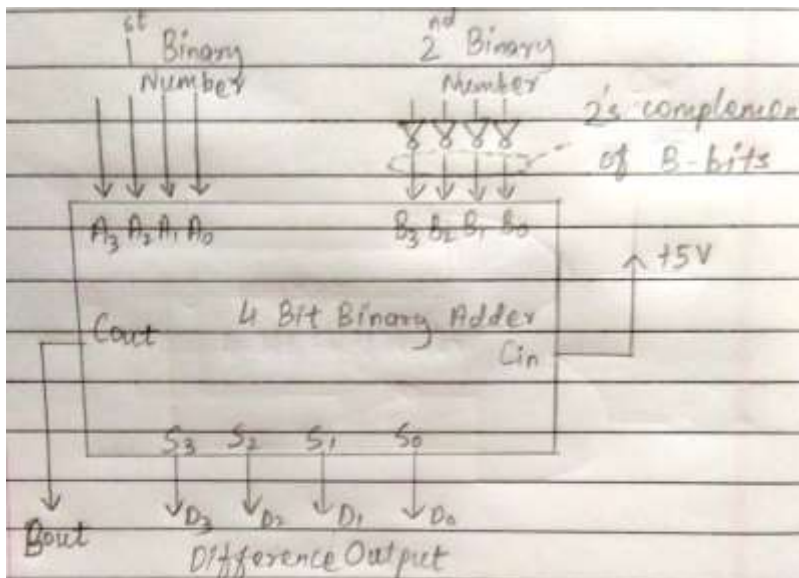

Post Lab Descriptive Questions:

1. What is difference between half and full adder, half and full subtractor?

Ans. **Full adder and half adder:**

The difference between half adder and full adder is that full adder has three inputs and two outputs. The two inputs are A and B and the third is a carry input C_{in} . The output carry is designated as C_{out} and the normal output is designated as S whereas half adder has two inputs and one output and carry is neglected in half adder. It isn't neglected in full adder.

Full subtractor and half adder:

The difference between half subtractor and half subtractor is also the same. Half subtractor has two inputs and one output while full subtractor has 3 inputs and 2 outputs and bits are borrowed in full subtractor. It is not restricted to one bit subtraction.



K. J. Somaiya College of Engineering, Mumbai-77

2. Perform the following Binary subtraction with the help of appropriate ICs:

- a) 7-5
- b) 5-7
- c) 9-4

Ans. a) The binary form of 7 is:0111

The binary form of 5 is: 0101

1's complement of 5 is:1010

 + 1

2's complement of 5 is:1011

Thus 7-5 is:

0111

+1011

$(0010)_2 = (2)_{10}$

b) The binary form of 5 is: 0101

The binary form of 7 is: 0111

1's complement of 7 is: 1000

 + 1

2's complement of 7 is: 1001

Thus 5-7 is:

0101

+1001

$(1110)_2$



K. J. Somaiya College of Engineering, Mumbai-77

The answer is a negative number. Hence we take the 2's complement

1's complement: 0001

+1

2's complement: $(0010)_2 = (2)_{10}$

c) The binary form of 9 is: 1001

The binary form of 4 is: 0100

1's complement of 4 is: 1011

+1

2's complement of 4 is: 1100

Thus 9-4 is:

1001

+1100

$(0101)_2 = (5)_{10}$

Conclusion:

The binary circuit for half/full adder and subtractor were studied by both basic gates and dedicated gates for various test cases with correct outputs.