



**K. J. Somaiya College of Engineering, Mumbai-77**

**Experiment / Assignment / Tutorial No. 4**

**Grade: AA / AB / BB / BC / CC / CD / DD**

**Signature of the Staff In-charge with date**

**K. J. Somaiya College of Engineering, Mumbai-77**

**Batch: B1**

**Roll No.: 1711072**

**Experiment / assignment / tutorial No.: 4**

**Title: 4 bit Magnitude Comparator**

**Objective:** Design a 2-bit comparator using logic gates and verify 4-bit magnitude comparator using IC 7485

**Expected Outcome of Experiment:**


**CO2:** Use different minimization technique and solve combinational circuits, synchronous & asynchronous sequential circuits.

**Books/ Journals/ Websites referred:**

- R. P. Jain, "Modern Digital Electronics", Tata McGraw Hill
- M. Morris Mano, "Digital Logic & computer Design", PHI
- [http://elnsite.teilam.gr/ebooks/digital\\_design/lab/dataSheets\\_page/7485.pdf](http://elnsite.teilam.gr/ebooks/digital_design/lab/dataSheets_page/7485.pdf)

 **Pre Lab/ Prior Concepts:**

The comparison of two numbers is an operator that determines one number is greater than, less than (or) equal to the other number. A magnitude comparator is a combinational circuit that compares two numbers A and B and determines their relative magnitude. The outcome of the comparator is specified by three binary variables that indicate whether  $A > B$ ,  $A = B$  (or)  $A < B$ .



## K. J. Somaiya College of Engineering, Mumbai-77

### Two Bit Magnitude Comparator Implementation Details:

#### Truth Table

A1	A0	B1	B0	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

From the Truth Table:


$$(A < B) = A_1' A_0' B_0 + A_1' B_1 + A_0' B_1 B_0$$

$$(A = B) = (A_1 \oplus B_1)(A_0 \oplus B_0)$$

$$(A > B) = A_0 B_1' B_0' + A_1 A_0 B_0' + A_1 B_1'$$


## K. J. Somaiya College of Engineering, Mumbai-77

### Logic Diagram of 2 bit Comparator

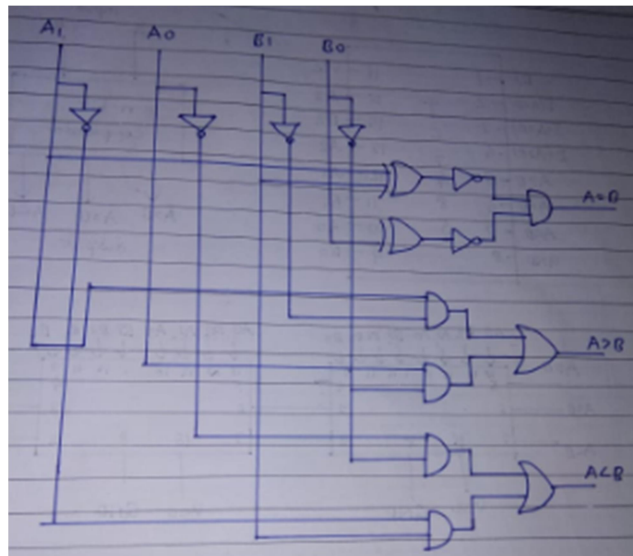


### Four Bit Magnitude Comparator Implementation Details

#### Pin Diagram of IC 7485

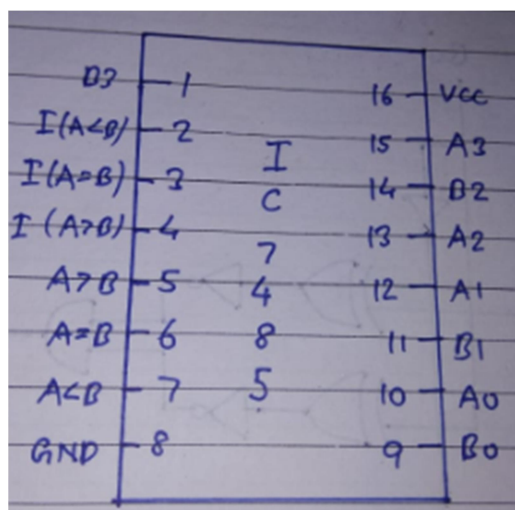

## K. J. Somaiya College of Engineering, Mumbai-77

### Logic Diagram of IC 7485

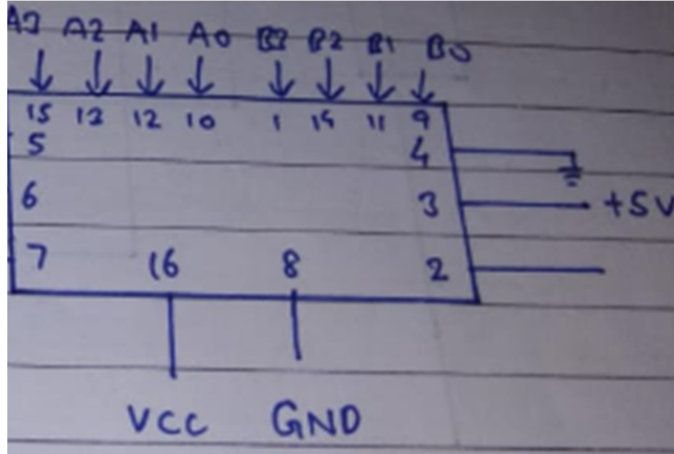

### Comparing Table

Comparing inputs								Cascading inputs			Outputs		
A3	B3	A2	B2	A1	B1	A0	B0	A>B	A<B	A=B	A>B	A<B	A=B
A3>B3		X		X		X		X	X	X	1	0	0
A3<B3		X		X		X		X	X	X	0	1	0
A3=B3		A2>B2		X		X		X	X	X	1	0	0
A3=B3		A2<B2		X		X		X	X	X	0	1	0
A3=B3		A2=B2		A1>B1		X		X	X	X	1	0	0
A3=B3		A2=B2		A1<B1		X		X	X	X	0	1	0
A3=B3		A2=B2		A1=B1		A0>B0		X	X	X	1	0	0
A3=B3		A2=B2		A1=B1		A0<B0		X	X	X	0	1	0
A3=B3		A2=B2		A1=B1		A0=B0		1	0	0	0	1	0
A3=B3		A2=B2		A1=B1		A0=B0		0	1	0	0	1	0

### K. J. Somaiya College of Engineering, Mumbai-77

A3=B3	A2=B2	A1=B1	A0=B0	0	0	1	0	0	1
A3=B3	A2=B2	A1=B1	A0=B0	X	X	1	0	0	1
A3=B3	A2=B2	A1=B1	A0=B0	1	1	0	0	0	0
A3=B3	A2=B2	A1=B1	A0=B0	0	0	0	1	1	0

#### Conclusion:

1-bit and 2-bit comparators were successfully designed using gates, whereas 4-bit comparator was verified successfully using IC 7485. We also learned that cascading can be done using (C 7485 for designing higher bits comparators like 8-bit and so on.

#### Post Lab Descriptive Questions

1. Design a 1- bit magnitude comparator using logic gates.

Ans.

